

# Hardware Design I Chap. 1

## Outline of LSI Design

Computing Architecture Lab.  
Hajime Shimada  
E-mail: shimada@is.naist.jp

1


## Outline of Chap. 1

- Definition of digital system
- History of digital system
  - From vacuum bulb to field effective transistor (FET)
- The physical image of current device
  - Metal Oxide Semiconductor (MOS) FET
  - CMOS organization (CMOS NAND, CMOS NOR)
- Outlined flow of LSI design
- Outlined flow of semiconductor process



 
## What is a digital system?

- The system which process information with digital notations
  - Usually implemented as **Large Scale Integration (LSI)**



 - The signal is digital (0/1)
- The signal state switches with the other signal value



## What is digital notation?

- It only allows two values: **0** or **1**
  - Discrete values -> manipulated under discrete mathematics rules (logical operation) -> Chap. 2
  - Easy to allocate **ON** or **OFF** status in electric circuits
- Suitable to current field effective transistor based electric circuits -> later Chap. 1
  - We can also implement same function with analog circuit, but it requires further costs
  - Analog value in practical world is translated via analog-digital converter (AD converter)
    - Also there's DA converter to translate processed result

## How to represent 0/1 in electric circuits

- We have to define representation on electric circuit
- In usual circuit, we use high/low voltage
  - 0: low voltage (conducted to ground)
  - 1: high voltage (conducted to power supply)
- The other representations
  - Current (relay)
  - Spin of electron (spintronics)
  - Single quantum flux (superconductive element)




## Outline of Chap. 1

- Definition of digital system
- History of digital system
  - From vacuum bulb to field effective transistor (FET)
- The physical image of current device
  - Metal Oxide Semiconductor (MOS) FET
  - CMOS organization (CMOS NAND, CMOS NOR)
- Outlined flow of LSI design
- Outlined flow of semiconductor process



 
# Relay: a primitive switch

- It can control current ON/OFF status by the other current
  - Utilize electromagnet to control output current
  - Represent 0/1 with current
    - 0: current does not flow
    - 1: current flows


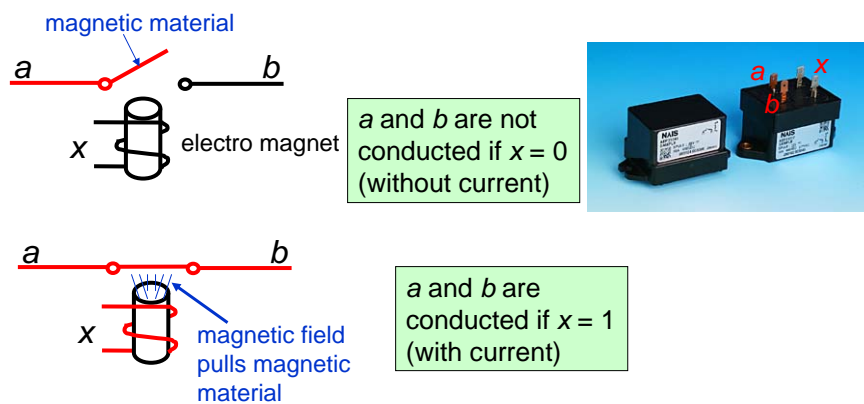
# Operation of the relay

- Open or close switch with the current supplied to electro magnet



## Sample basic logic operation

- Let's achieve these operation with relay

- Logical product (AND)

- Output becomes 1 if both of two input is 1
- Otherwise output is 0

- Logical addition (OR)

- Output becomes 1 if either of two input is 1
- Otherwise output is 0

- Negation (NOT)

- Output becomes 0 if input is 1
- Output becomes 1 if input is 0


Detail of logic operation  
-> Chap. 2 and 3



## Logical function with relay (1/2)


- We can represent logic function by relay

NOT function:  $\bar{x}$  or  $x'$

 

$a$  and  $b$  are conducted if  $x = 0$  and not conducted if  $x = 1$  (inverse action)


AND function:  $x \cdot y$

 

## Logical function with relay (2/2)


- We can represent logic function by relay

OR function:  $x + y$

 
 
## Computer constructed with relay

- Harvard Mark I (1944)
  - Utilizes about 3,300 relays
  - Operate multiply in 5.7 sec. and division in 15.3 sec.



 
## Transition of switch





Relay

- Mechanical abrasion makes it broken
- Operation speed limit from physical behavior



Vacuum bulb

  - Breaks as well as lamp bulb
- Used around 1940s to 1950s



Transistor

- **Hard to break**
- Still integrated even in latest ULSI
- Used after 1950s



## Quiz

- What is the first computer in the world (using vacuum bulb)?
  1. ENIVAC
  2. ENIAC
  3. EDSAC
  4. EDVAC
- Note that there's some "the first computer" candidates, but please choose most famous one



## Answer

- 2. **“ENIAC”**
  - Other candidates: Atanasoff-Berry Computer, Zuse Z3
- 3. **“EDSAC”** is also famous as a the first “neuman type computer”
  - Other candidates: Manchester SSEM



## Outline of Chap. 1


- Definition of digital system
- History of digital system
  - From vacuum bulb to field effective transistor (FET)
- The physical image of current device
  - Metal Oxide Semiconductor (MOS) FET
  - CMOS organization (CMOS NAND, CMOS NOR)
- Outlined flow of LSI design
- Outlined flow of semiconductor process





# Semiconductor

Si (silicon) has 4 valence electrons

 


- Half conduct the electric current
  - Usually, there's no free electron
  - By adding voltage (over threshold), the electron can move
- If we dope some impurity, the conductivity increases dramatically



# Hole and free electron

Free electron

Hole

 


- Voltage load sometimes moves electron and creates hole and free electron
  - Hole: A space which electron has existed
  - Free electron: A electron which can move freely


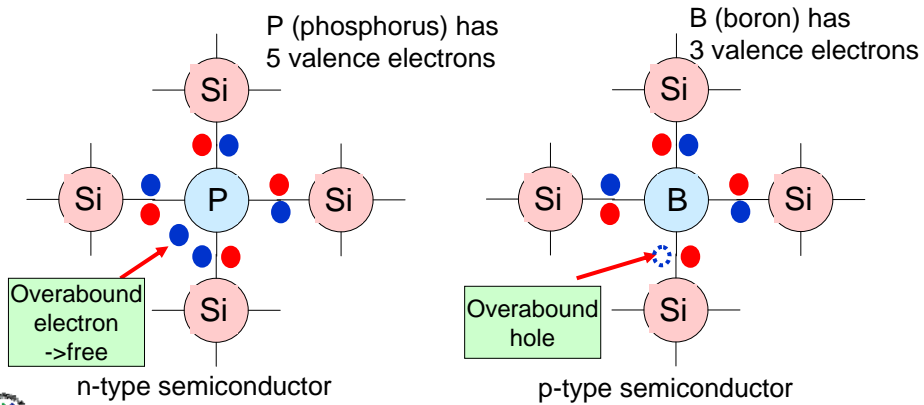
# Impurity semiconductor

- Doped impurity creates overabundant electron or hole
- Additional electron or hole carries current




Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

19
 
# Current flow of n-type semiconductor

- The movement of free electrons create current




Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

20
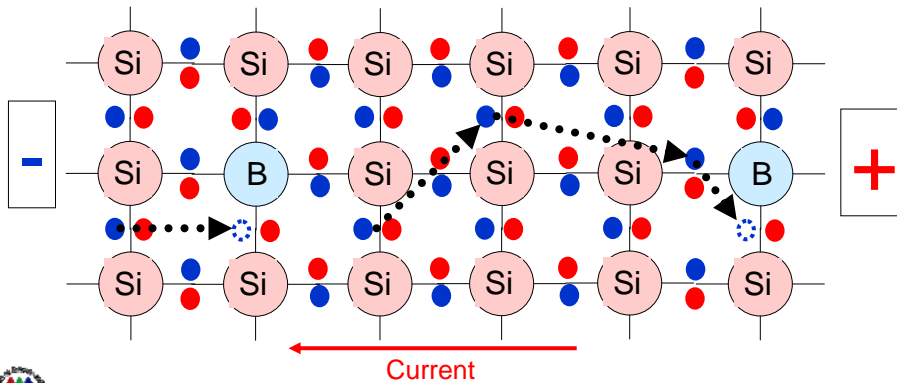
## Current flow of p-type semiconductor

- The movement of hole create current
  - The fixed electron moves and trapped at hole
    - >The hole moves to the point where the electron has existed



Computing Architecture Lab.  
Hajime Shimada



Hardware Design I (Chap. 1)

21

## nMOS field effect transistor (FET)

- If we add voltage to **gate**, electrons gather under dielectric
  - It creates n-channel
- >Current flows from drain to source

Circuit symbol

  


Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)


22

## Operation of nMOS FET

- OFF state

 

- On state

 

n-channel (flood with electron) has created




## Why it called MOS transistor?

- **M**etal
  - Aluminum (traditional), copper (current)
- **O**xide
  - SiO<sub>2</sub> (traditional), HfON (current high-end)
- **S**emiconductor
  - Silicon
  - In the future: carbon nano tube???



 
## Digital (0/1) notation with FET

- 0 state is denoted with the voltage of ground (0V)
- 1 state is denoted with the voltage of supply voltage (5V, 3.3V, 2.5V, 1.8V, 1.5V, and so on)
  - Denoted as Vcc or Vdd
  - Vdd differs in semiconductor process technology



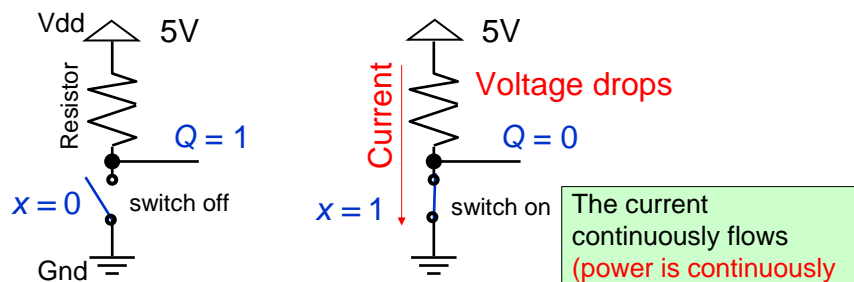
## Creating NOT logic with switch

- NOT logic
  - Assuming 1 input  $x$  and 1 output  $Q$
  - $Q = x'$  (negative value of  $x$ )
- Let's create it with switch



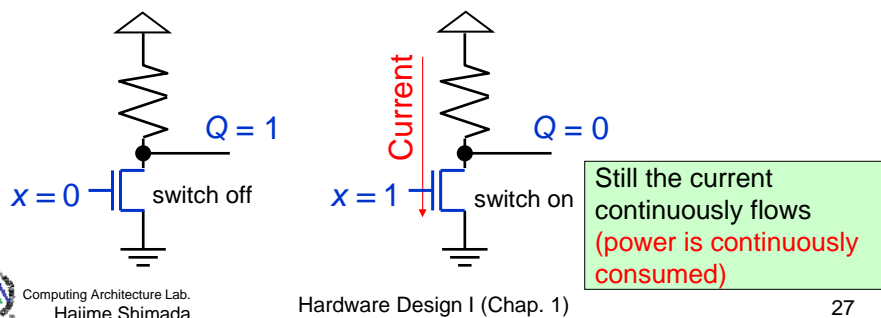
## Creating NOT logic with nMOS FET

- We can replace switch to nMOS FET
  - This is an ancient implementation to save number of FET
- Problem of this organization
  - Consumes huge power
  - Next step: let's eliminate continuous current


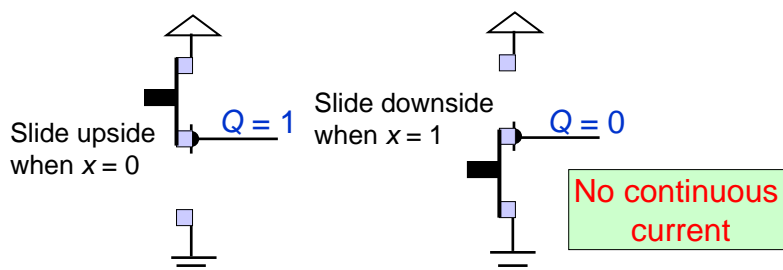
## NOT logic with slide switch



- Let assume slide switch
- It does not consume energy in steady state
- Next step: let's create slide switch with MOS



# pMOS field effect transistor (FET)

- pMOS FET which has opposite characteristic to nMOS FET
- If we add voltage to gate, holes under dielectric banish

Circuit symbol

  


Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)


29
 
# Operation of pMOS FET

- OFF state
  - Channel disappears when the voltage has applied Gate



- On state

 

p-channel (flood with hole) has created



Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

30

# nMOS and pMOS



## nMOS FET

- OFF state if input is 0
- ON state if input is 1
- The carrier is electron

## pMOS FET


- OFF state if input is 1
- ON state if input is 0
- The carrier is hole
- Maximum current is half of that of nMOS

We can prepare complementally switch

  

 
# CMOS NOT logic

- CMOS: Complementary MOS
  - Combines nMOS and pMOS
- **Does not consume energy in steady state**



Upside is ON,  
downside is OFF

 

Upside is OFF,  
downside is ON





 
## Basic of power consumption on CMOS logic

- In CMOS circuit, charge moves to Gnd with following procedure
  - Charge moves to Vdd to output node with input 0
  - Charge moves to output node to Gnd with input 1

0 → 1 → 0 transition makes **one unit of power consumption**



## Equation of CMOS power consumption


$$\text{Power} \propto C \times F \times V^2$$

- C: Capacitance
  - Capacitance of output node
  - Internal FET capacitance
- F: Frequency
  - Clock frequency in synchronous circuit
  - Otherwise, number of switching
- V: Supply voltage



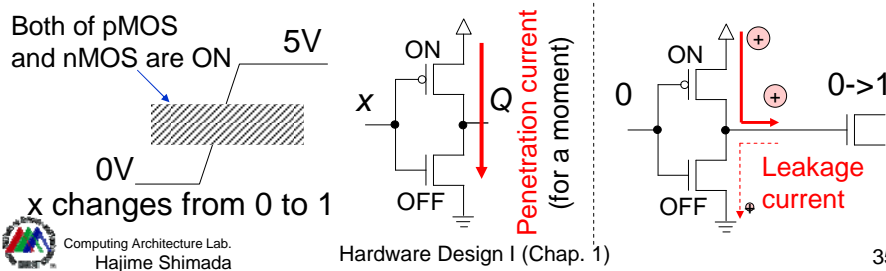
## Power consumption in CMOS NOT logic (Advancement)

- Penetration current under transition
  - Both pMOS and nMOS conducts for a moment
- Leakage current
  - Few current flows even in OFF state
  - Let assume the faucet which cannot fully close and leaks water


 
## CMOS NAND and NOR


- 2 input NAND (NOT AND)
  - $Q = 0$  if both  $x$  and  $y$  is 1, otherwise  $Q = 1$
- 2 input NOR (NOT OR)
  - $Q = 1$  if both  $x$  and  $y$  is 0, otherwise  $Q = 0$



We can create logic gate by combining FET

 
# Water pressure logic

- Let's create logic in some other material
- e.g. water pressure logic
  - Create pMOS and nMOS like water valve
  - They operate with input side water pressure


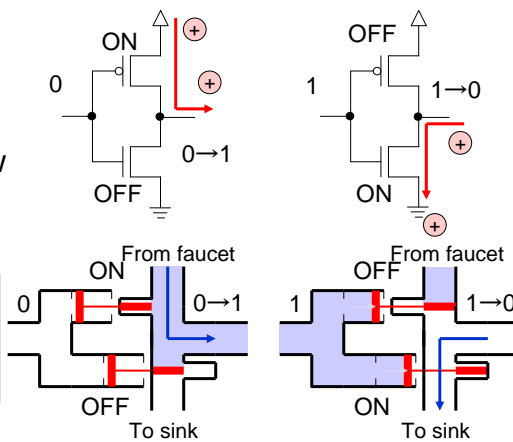
# Water pressure NOT logic

- Combining valve to create NOT logic
  - Vdd = faucet
  - Gnd = sink
  - Current = water flow



If we create some operateable logic with it, I think that it becomes good art work



## Outline of Chap. 1

- Definition of digital system
- History of digital system
  - From vacuum bulb to field effective transistor (FET)
- The physical image of current device
  - Metal Oxide Semiconductor (MOS) FET
  - CMOS organization (CMOS NAND, CMOS NOR)
- Outlined flow of LSI design
- Outlined flow of semiconductor process



## About integrated circuits (1/2)

- Semiconductor technology allows integrating many transistors into one silicon chip
- Level of integration
  - Integrated circuit (IC): less than 1000 transistors
  - Large scale integration (LSI): thousands to 10 thousands transistors



Logic IC TTL7400 (8 Tr)



Microcontroller  
STM32F103 (33,000 Tr)



## About integrated circuits (2/2)

- Level of integration
  - Very Large scale integration (VLSI): more than 100 thousand transistors
  - Ultra Large scale integration (ULSI): more than 1 million transistors
  - There's no name after ULSI



Embedded processor  
PXA270 (200 thousands Tr)



Processor for PC  
Intel Atom (46 millions Tr)



## Quiz

- How many transistors does latest LSI have?
  1. 100 millions transistors
  2. 300 millions transistors
  3. 1 billion transistors
  4. 3 billions transistors



## Answer

- 4. “3 billion transistors”

- Latest Intel Xeon has nearly 3 billions transistors
- But many of them are used for cache SRAM

SRAM -> Chap. 5

Cache -> Chap. 11, 12



## How to create such a LSI?

- Placing such a many transistors with hand designing is almost impossible



- Computer assistance is required
  - Computer Aided Design (CAD)
  - Design Automation (DA)
  - Electronic Design Automation (EDA)

In this lecture, I treat “the basic point of EDA”



## Outlined flow of LSI design

- Define specification -> Chap. 11, 12
- Definition in hardware description language
  - Architectural design -> Chap. 4, 5, 6, 11, 12
- ↓ Logic synthesis
- Circuit with basic logic gates
  - Logical design -> Chap. 2, 3, 4, 5, 7, 8
- ↓ Place and route
- Mask pattern
  - Physical design -> Chap. 9, 10
- Manufacturing



## Definition in Hardware Description Language (HDL)

- e.g. Definition of chronograph with Verilog HDL


```
module stopwatch(reset,clock,switch,sec1_lap,sec2_lap,min_lap,lap);
input reset,clock,switch,lap;
output [3:0] sec1_lap;
output [3:0] sec2_lap;
output [3:0] min_lap;

reg[3:0] sec1; // 10sinn
...
always @ (posedge clock or negedge reset ) begin
    if(reset == 1'b0) begin
        sec1_lap <= 4'b0000;
        lap_state <= L1;
    ...
endmodule
```

-> Chap. 4, 5, 6, 11, 12



## Circuit diagram after logic synthesis

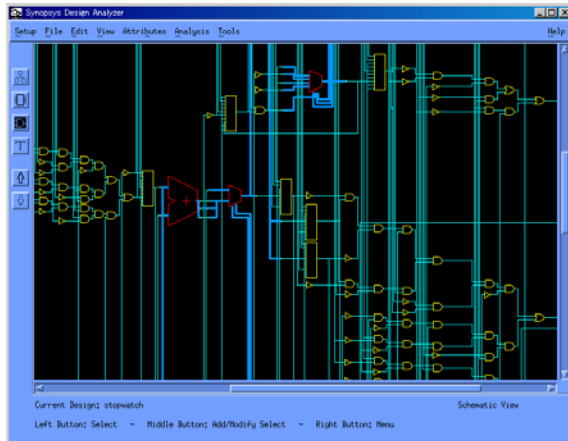


- Represented as Register Transfer Level (RTL) notation
- The circuit is denoted with logic gate symbols and wire connection

-> Chap. 2, 3, 4, 5, 7, 8




## Outline of logic gate symbol

 



## Place and route (1/2)

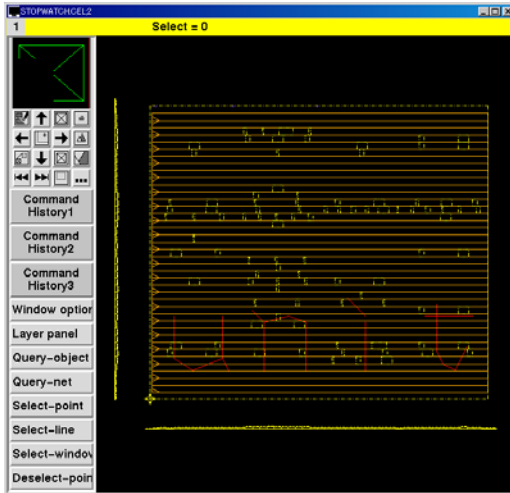


- Place logic cells into virtual silicon surface
- Each logic cell has designed in fix height and arbitrary diameter of unit width

-> Chap. 9, 10



## Place and route (2/2)

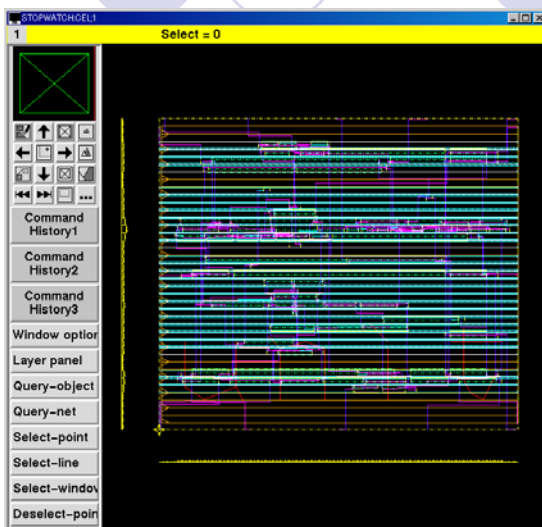


- Routing wires which connects logic cells

-> Chap. 9, 10



## Layout of designed LSI

 

- Including pin layout for external connection

-> later Chap. 1



## Outline of Chap. 1

- Definition of digital system
- History of digital system
  - From vacuum bulb to field effective transistor (FET)
- The physical image of current device
  - Metal Oxide Semiconductor (MOS) FET
  - CMOS organization (CMOS NAND, CMOS NOR)
- Outlined flow of LSI design
- Outlined flow of semiconductor process




# How to create CMOS

Final exterior



• By repeating following operation on silicon substrate

 - Injecting impurity
- Deposit silicon or metal
- Etch unnecessary area
- etc.




Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)


53

## Creating SiO<sub>2</sub> coat and prepare for etching

• Oxidate the surface of silicon

 

• Embrocate photo resist

 


Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

54
 
# Exposure

- Expose ultra violet ray under mask
  - Requires 7-10 masks in total (2-3M yen per 1 mask)
  - Latest process uses 193nm ultra violet ray
- Exposed area becomes hard




Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

55
 
# Etching

- Etches not harden photo resist and  $\text{SiO}_2$ 
  - Dry etching: etches with gas
  - Wet etching: etches with drug solution
- After that, harden photo resist is removed





Computing Architecture Lab.  
Hajime Shimada

Hardware Design I (Chap. 1)

56

## Creating p-well and ...

- Inject p-type impurity

 
 


- Embrocate photo resist and expose
- Inject n-type impurity
- Dope poly silicon
- ...



  
## Create pMOS and nMOS

- After several processes...
- pMOS and nMOS transistor has created on the silicon surface


 
## Create wire

- Create wire which conducts MOS transistors
  - Aluminum wire (traditional) or copper wire
- Finally we can create logic gates (or circuits) on the silicon surface



## Advancement with shrinking

- Semiconductor advances with shrinking minimum process width
  - Enables much transistors into same size
  - Enables quick operation with reduces capacitance
- Industries shrinks it every 2 or 3 years
  - e.g. Intel's process technology: 90nm (2004), 65nm (2006), 45nm(2008), 32nm(2010)
- But physical bound is very close
  - Atom is countable even in current process technology
  - Do we have to move to the other devices?

