

Hardware Design I Chap. 2

Basis of logical circuit, logical expression, and logical function

Computing Architecture Lab.
Hajime Shimada
E-mail: shimada@is.naist.jp

1

Outline

- Combinational logical circuit
 - Logic gate (logic element)
 - Definition of combinational logical circuit
 - How to create output signal?
- Logical function
 - Definition of logical function
 - Relationship between logical circuit
- Logical expression
 - Definition of logical expression
 - Minterm and maxterm
 - Axiomatic systems
 - Amount of logical expression




Review: outlined flow of LSI design

- Define specification
- Definition in hardware description language
 - Architectural design
- ↓ Logic synthesis
- Circuit with basic logic gates
 - Logical design ← This chapter treats this area
 - Logical function
 - Logical expression
- ↓ Place and route
- Mask pattern
 - Physical design
- Manufacturing



Relationship between technical terms

Specification

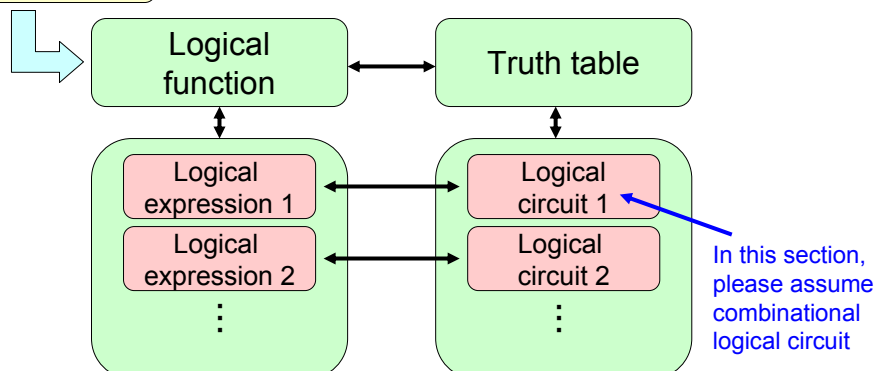

- If we minimize logical expression, we can implement minimized logical circuit



Detailed talk of logical design

- Specification of sequential machine -> Chap. 6
- ↓
- Specification of logical function -> later Chap. 2
- ↓
- Logical expression -> later Chap. 2
 - Simplify of two level logic -> Chap. 3 and 7
 - Simplify of multi level logic -> Chap. 7 and 8
- ↓
- Simplified logical expression
= Basic logic gates




Logic gate (logic element)

- The electric circuit with outputs result of logical operation
 - e.g. NOT, NAND
 - Both inputs and outputs can only take 0 or 1


NOT gate

Circuit symbol

 

NAND gate

Circuit symbol

 


-> Chap. 1



NOT, AND, and OR on Boolean algebra

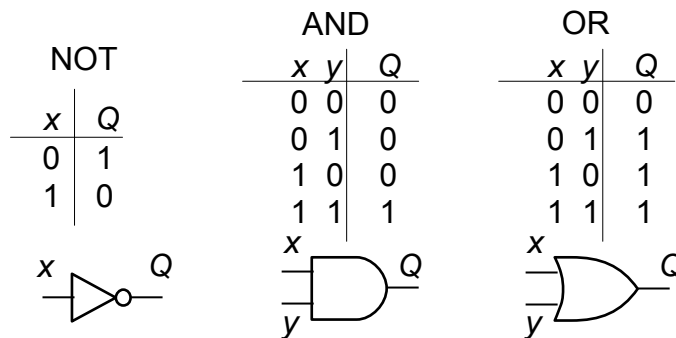- Logical circuit operates on Boolean algebra
- Here's basic logic from Boolean algebra




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

7

NOT, AND, and OR on Venn diagram

 - In some case, imaging Venn diagram helps understanding
 - NOT: left area
 - AND: shared area
 - OR: sum of area



Computing Architecture Lab.
Hajime Shimada


Hardware Design I (Chap. 2)

8



NAND and NOR on Boolean algebra

- Physical implementation is easy -> Chap. 1
- Usually, AND and OR are implemented by combining NOT and NAND/NOR

NAND		
x	y	Q
0	0	1
0	1	1
1	0	1
1	1	0

 

NOR		
x	y	Q
0	0	1
0	1	0
1	0	0
1	1	0

  


Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

9

Combinational logical circuit

 - The signal flow must be contra flow
- The output of the gate will be defined from input side
- The output is defined with current input
 - No loop in it
 - It is also called "acyclic circuit"




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)


10

Let's assume looped logic circuit (1/2)

 - It sometimes gives unstable output
 - Let's assume 1 is inputted under 0 output status



 - Let's assume 1 is inputted under 1 output status




The output switches 0/1 forever!!! ->oscillator




Let's assume looped logic circuit (2/2)

- We rarely achieve stable circuit with looped combinational circuit

 - Let's assume 1 is inputted under 1 output status
 - It continues to output 1



 - Once input falls to 0, the output changes to 0 forever




Usually, they are rare and utilization is limited...

How to create loop?
-> Sequential circuit
(Chap. 6)



Definition of combinational logic with directed graph

 - Set of vertices: $V=\{a, b, c, d, e, f, g, h\}$
- Set of edges: $E\subseteq(V\times V)$
 $E=\{(a,e), (b,e), (b,d), (c,f), (d,f), (e,g), (f,g), (g,h)\}$
- Label of vertex: NOT, NAND, and so on



If you felt “what is directed graph?” ...

- Please relearn “graph theory”
 - The sets of vertices and edges
 - e.g. network connection graph, schematic diagram, ...
 - Specific graph: tree, directed graph, weighted graph, ...
- It is widely used in informatics world
 - Syntax tree (compiler)
 - Markov chain (voice recognition)
 - Perceptron (neural network)



About technical terms of set theory

- Set
 - Gathered set of elements
 - e.g. $\{0, 1\}$, $\{a, b, \dots, z\}$, ...
- Cartesian product
 - A set of ordered pairs of elements
 - Notation: $A \times B$ (A,B: set)
 - e.g. $\{0, 1\} \times \{a, b\} = \{(0,a), (0,b), (1,a), (1,b)\}$
 - Other notation: V^2 , $\{0, 1\}^2$




The syntax of combinational logic from graph theory

- **Directed Acyclic Graph (DAG): (V, E)**
 - V: set of vertices
 - E: set of edges, subset of $(V \times V)$
 - $(V \times V)$ denotes set of Cartesian product
- Allocate logic gate (e.g. NAND) label to vertices
 - Allocate 1 label to 1 vertex




Terms of combinational logic (1/3)

 - Fan-in: a input side of edge
 - e.g. v_1 is the fan-in of edge (v_1, v_2)
 - Viewpoint from the v_2 side
- Fan-out: a output side of edge (v_1, v_2)
 - e.g. v_2 is the fan-out of edge (v_1, v_2)



Terms of combinational logic (2/3)

 - Primary input: a vertex which does not have fan-in
- Primary output: a vertex which does not have fan-out




Terms of combinational logic (3/3)

- Path: a set of edges from primary input to primary output

- e.g. $(v_1, v_2) (v_2, v_3) \dots (v_{n-1}, v_n)$

- v_1 is transitive fan-in

- v_n is transitive fan-out

 


Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

19

Value allocation to logic circuit

 - Value allocation
 - Allocate 0/1 value to (output of) each vertex
 - Adequate allocation: satisfies the truth of gate
- The allocation will be defined if all of primary input has defined
- It is also called **logic simulation**



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

20


The algorithm of value allocation

1. Define the value of primary inputs
 - Primary inputs are called **level 0 vertices**
2. Define the value of level 1 vertices
 - Level 1 vertices: all inputs of them are primary input
 - All inputs value are already defined in 1.
3. Define the value of level 2 vertices
 - Level 2 vertices: all inputs of them are less than level 1 (level 0 or 1)
4. Define level n vertices until the all of the vertices have defined
 - Level n vertices: all inputs of them are less than level n-1



 
Example of value allocation (1/4)

- Allocate value to primary inputs (level 0 vertices)
 - We can allocate them without constraint
 - Usually, they are given



 Example of value allocation (2/4)

- Allocate values to level 1 vertices
 - Which are only connected to primary inputs




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

23

 Example of value allocation (3/4)

- Allocate values to level 2 vertices
 - Which are only connected to less than level 1 vertices
 - See the vertices which values have already allocated




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

24

 
Example of value allocation (4/4)

- Allocate value to level 3 vertices
 - Which are only connected to less than level 2 vertices
 - The allocation of primary outputs are the same to the prior vertices




Short exercise

 - Allocate values to left vertices
 - If you left time, add level notations to the vertices



The answer of short exercise

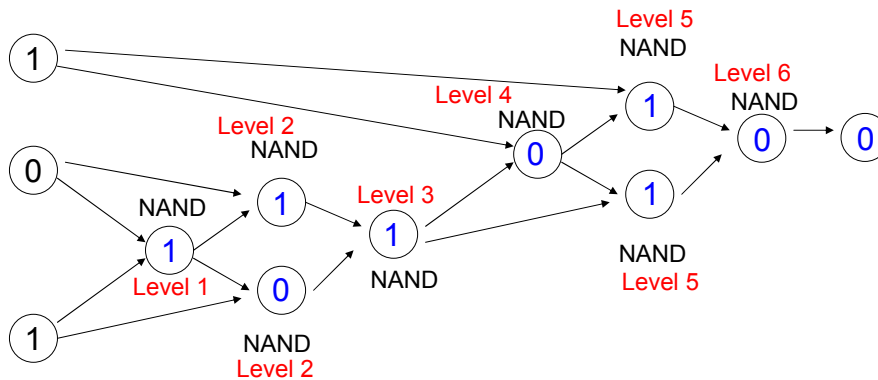

Outline

- Combinational logical circuit
 - Logic gate (logic element)
 - Definition of combinational logical circuit
 - How to create output signal?
- Logical function
 - Definition of logical function
 - Relationship between logical circuit
- Logical expression
 - Definition of logical expression
 - Minterm and maxterm
 - Axiomatic systems
 - Amount of logical expression



Definition of logical function from mathematical viewpoint

- Representation of the relationship between input value and output value
- The definition of n -value logical function:


Projection from $\{0, 1\}^n$ to $\{0, 1\}$

- Subset $f \subseteq \{0, 1\}^n \times \{0, 1\}$ which does not include both $(X, 0) \in f$ and $(X, 1) \in f$ in arbitrary X
- We denote it $y = f(X)$ if $(X, y) \in f$
- $\{0, 1\}^n$ is called domain
- $\{0, 1\}$ is called codomain



 Example of definition of 3-value logical function (notated by logical circuit)

- It outputs 0 if we input (0, 0, 0) into it
 - It outputs 1 if we input (0, 0, 1) into it
 - \vdots
 - It outputs 1 if we input (1, 1, 1) into it
- } This is logical function!



Examples of definition of representative logical function

- The function of NOT $\subseteq \{0,1\} \times \{0,1\}$
 - $\{(0, 1), (1, 0)\}$
- The function of AND $\subseteq \{0,1\}^2 \times \{0,1\}$
 - $\{((0, 0), 0), ((0, 1), 0), ((1, 0), 0), ((1, 1), 1)\}$
- The function of AND $\subseteq \{0,1\}^2 \times \{0,1\}$
 - $\{((0, 0), 0), ((0, 1), 1), ((1, 0), 1), ((1, 1), 1)\}$
 - Input Output



How to denote them in usual?

- Usually, we do not use mathematical definition
- We usually use following notations
 - Logical circuit
 - Truth table
 - Logical expression



Truth table

- One of the representation style of logical function
- Aligning output values for all possible inputs
- The size of n values logical function is 2^n

x_1	x_2	$f(x_1, x_2)$	$g(x_1, x_2)$	$h(x_1, x_2)$
0	0	0	0	$h(0, 0)$
0	1	0	1	$h(0, 1)$
1	0	0	1	$h(1, 0)$
1	1	1	0	$h(1, 1)$

If truth tables of two functions are identical, the functions are identical

Logical function

One for one relationship

Truth table




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

33

Relationship between logical function and logical circuit

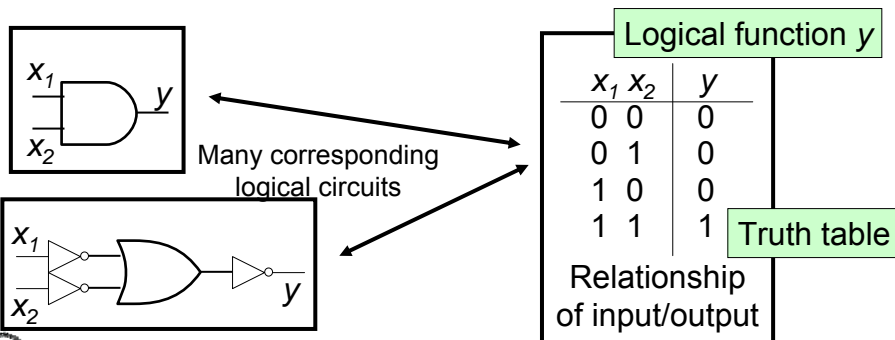- Logical function represents the relationship of input value and output value in combinational logical circuit




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

34

Relationship between technical terms

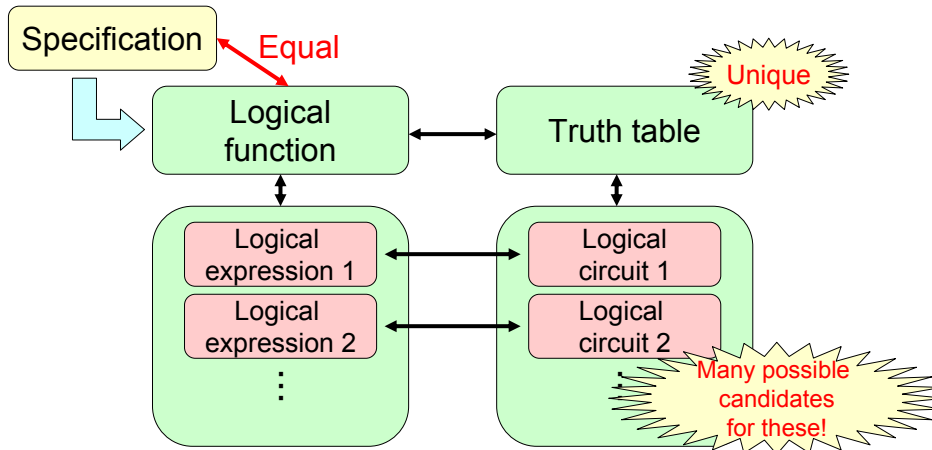


- If we minimize logical expression, we can implement minimized logical circuit



Multiple output logical function

 - In many case, digital system has multiple outputs
- Usually, we decompose it to multiple single output function for simplicity



Truth table of multiple output logical function

- Multiple output function (m outputs):

Projection from $\{0, 1\}^n$ to $\{0, 1\}^m$

- List of m projections from $\{0, 1\}^n$ to $\{0, 1\}$

x_1	x_2	$f_0(x_1, x_2)$	$f_1(x_1, x_2)$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



Operation between logical functions

- We can extend operation on logical value to logical function

- $(f \cdot g)(x_1, x_2, \dots, x_n) = f(x_1, \dots, x_n) \cdot g(x_1, \dots, x_n)$

- $(f + g)(x_1, x_2, \dots, x_n) = f(x_1, \dots, x_n) + g(x_1, \dots, x_n)$


- $(f^c)(x_1, x_2, \dots, x_n) = f(x_1, x_2, \dots, x_n)^c$

- Detail is taught in following logical expression section



Summary of logical function

 - It is a function from $\{0, 1\}^n$ to $\{0, 1\}$
 - $\{0, 1\}^n \times \{0, 1\}$ with some constraint
- It is represented uniquely with truth table
 - List of relationship between all inputs and outputs
 - But it requires 2^n size of memory
- We can apply operation on it



Logical function:
The relationship between
inputs and outputs





Outline

- Combinational logical circuit
 - Logic gate (logic element)
 - Definition of combinational logical circuit
 - How to create output signal?
- Logical function
 - Definition of logical function
 - Relationship between logical circuit
- Logical expression
 - Definition of logical expression
 - Minterm and maxterm
 - Axiomatic systems
 - Amount of logical expression



Logical expression

  - One of the expression of logical function
 - Represent it with arrangement of variable which denotes logical function
 - e.g. $x + y \cdot z + x \cdot y' \cdot z'$
- Efficient than truth table
- But there's no uniqueness
- $x = a+b; y = c \cdot d; z = x+y \rightarrow z = (a+b) + (c \cdot d)$



The definition of logical expression

1. Logical variables are logical expression
 - e.g. $x, y, z, x_1, x_2, a, b, \dots$
 2. If E_1 and E_2 are logical expression,
 - $(E_1 \cdot E_2), (E_1 + E_2), (E_1')$ are logical expression
 - e.g. $(x \cdot y), (x+y), (x+(y \cdot z)), (x+(y'))$
- Generated in recursively
 - We can omit brackets by adding order to operations
 - Order: $'$, \cdot , and $+$



The expression of logical function with logical expression (1/2)

- Pay attention to the logical function which has only one “1” output in truth table
 - Called **minterm**
 - Minterm can be represented by AND and NOT

Minterm

$x\ y$	$x' \cdot y'$	$x' \cdot y$	$x \cdot y'$	$x \cdot y$
0 0	1	0	0	0
0 1	0	1	0	0
1 0	0	0	1	0
1 1	0	0	0	1



The expression of logical function with logical expression (2/2)

- The logical function which has multiple “1” output is represented by OR of minterms
- The arbitrary function can be represented with AND, OR, and NOT of logical variable

Minterm


$x\ y$	$x' \cdot y'$	$x' \cdot y$	$x \cdot y'$	$x \cdot y$	$f(x,y) = x' \cdot y + x \cdot y'$
0 0	1	0	0	0	0
0 1	0	1	0	0	1
1 0	0	0	1	0	1
1 1	0	0	0	1	0




Notation only 2-input NAND or NOR

- We can represent NOT, AND, and OR with NAND gates by following wire connection
 - Called “NAND has **functional completeness**”
- Similar representation can be done with only NOR gates


NOT with NAND

 

AND with NAND

 

OR with NAND

 

See De Morgan's law in later



Sum of products

- Definition
 - Literal: Logical value or the negation of logical value
 - a: positive literal
 - a': negative literal
 - 1. Create term with AND of literals
 - 2. Create logical expression with OR of 1.
- e.g. $abc + a'b'c + ac$, $ac + bc + ad'e$
- Other names: AND-OR type, two level logic
- The **sum of minterms** has special name
 - > **Disjunctive Normal Form (DNF)**



Disjunctive Normal Form (DNF)

- Sum of minterms **without same minterm**

○ Arbitrary logical function can be expressed with DNF

a	b	f	g
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$f = a'b + ab'$$

$$g = a'b' + ab$$

a	b	c	h	s	t
0	0	0	0	0	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	0	1	1

$$h = a'b'c + a'bc + ab'c + abc'$$

$$s = a'b'c + a'bc + ab'c + abc$$

$$t = a'b'c' + a'b'c + abc' + abc$$



Product of sums

- Definition

- Create term with OR of literals
- Create logical expression with AND of 1.

- e.g. $(a+b'+c)(a'+b+c)(d+e')$

- There's a counterpart notation of DNF

-> **Conjunctive Normal Form (CNF)**

○ **Sum of maxterms**

○ **Maxterm**: the logical function which has only one "0" output in truth table



Maxterm

- Pay attention to the logical function which has only one "0" output in truth table
 - Called **maxterm**
 - Maxterm can be represented by OR and NOT

Maxterm

$x\ y$	$x+y$	$x+y'$	$x'+y$	$x'+y'$	$f(x,y) = (x+y)(x'+y')$
0 0	0	1	1	1	0
0 1	1	0	1	1	1
1 0	1	1	0	1	1
1 1	1	1	1	0	0



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

49

Conjunctive Normal Form (CNF)

- Sum of maxterms **without same maxterm**
 - Arbitrary logical function can be expressed with CNF

$a\ b$	$f\ g$	$a\ b\ c$	$h\ s\ t$
0 0	$a'b'$ 0 1	0 0 0	$a'b'c'$ 0 0 1
0 1	$a'b$ 1 0	0 0 1	$a'b'c$ 1 1 1
1 0	ab' 1 0	0 1 0	$a'bc'$ 0 0 0
1 1	ab 0 1	0 1 1	$a'bc$ 1 1 0
		1 0 0	$ab'c'$ 0 0 0
		1 0 1	$ab'c$ 1 1 0
		1 1 0	abc' 1 0 1
		1 1 1	abc 0 1 1

$$f = (a'+b')(a+b)$$

$$g = (a'+b)(a+b')$$

$$h = (a+b+c)(a+b'+c)(a'+b+c)(a'+b'+c')$$

$$s = (a+b+c)(a+b'+c)(a'+b+c)(a'+b'+c)$$

$$t = (a+b'+c)(a+b'+c')(a'+b+c)(a'+b+c')$$




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

50

Symbol simulation

 - A method to obtain logical expression from logical circuit
- Propagate symbol from inputs
 - Operate expression from lower level
 - > Similar to value allocation



Simplify with operation on Boolean algebra

- The logical expression given from symbol simulation has complexity
 - e.g. $((a \cdot b)' \cdot (b' \cdot c))'$
- How to simplify them?
 - ↓
- Simplify with operation on Boolean algebra
 - General operation rule
 - De Morgan's law
 - Shannon's expansion





Axiomatic systems related simplification on Boolean algebra

- General operation rules

- Idempotent: $a+a = a$
- Commutativity: $a+b = b+a$
- Associativity: $(a+b)+c = a+(b+c)$
- Absorption: $a+(a \cdot b) = a$
- Distributive: $(a+b) \cdot c = a \cdot c + b \cdot c$
- Involution: $(a')' = a$
- Complements: $a+a' = 1$
- Identity: $a \cdot 1 = a$
- Domination: $a \cdot 0 = 0$
- De Morgan's law: $(a+b)' = a' \cdot b'$

Venn diagram

  

Axiomatic systems related simplification on Boolean algebra

- Duality

- The rule that exchanged “+ and \cdot ” and “0 and 1” will be approved (Dual rule)
- e.g. $a+a = a \longleftrightarrow a \cdot a = a$
- e.g. $a+a' = 1 \longleftrightarrow a \cdot a' = 0$

- We can insert arbitrary logical expressions into a, b, and c in prior equations



Review: 2-input logical operation

- AND, OR, NAND, and NOR: described before
- XOR: output 1 if the inputs are not equal
- XNOR: output 1 if the inputs are equal

x y	AND $x \cdot y$	OR $x + y$	NAND $(x \cdot y)'$	NOR $(x + y)'$	XOR $x \oplus y$	XNOR $(x \oplus y)'$
0 0	0	0	1	1	0	1
0 1	0	1	1	0	1	0
1 0	0	1	1	0	1	0
1 1	1	1	0	0	0	1



De Morgan's law

- $(x \cdot y)' = x' + y'$
- $(x + y)' = x' \cdot y'$
- We can insert arbitrary logical expressions into x and y

x y	$(x \cdot y)'$	$x' + y'$	$(x + y)'$	$x' \cdot y'$
0 0	1	1	1	1
0 1	1	1	0	0
1 0	1	1	0	0
1 1	0	0	0	0


Equal

Equal



De Morgan's law on Venn diagram

 - Here's $(x \cdot y)' = x' + y'$ on Venn diagram



De Morgan's law on circuit level

- NAND and NOR becomes AND and OR with negated inputs

- $(x \cdot y)' = x' + y'$




- $(x + y)' = x' \cdot y'$



A practical use of De Morgan's law on circuit level

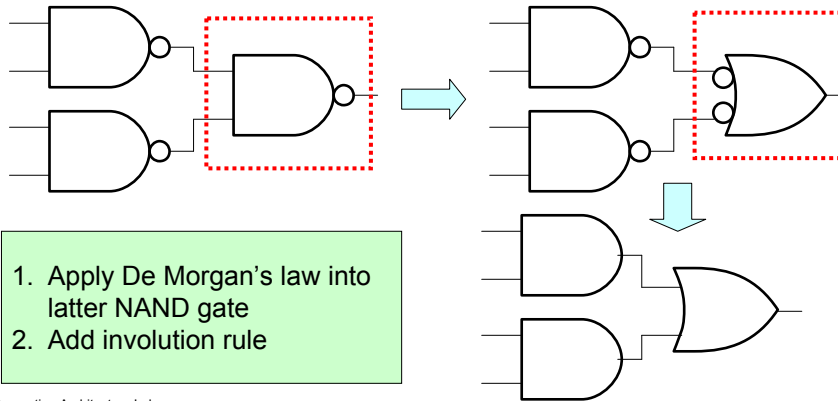- NAND-NAND two level logic circuit
= AND-OR two level logic circuit



1. Apply De Morgan's law into latter NAND gate
2. Add involution rule



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

59

Generalized De Morgan's law

$$F'(x_1, x_2, \dots, x_n) = G(x_1, x_2, \dots, x_n)$$

Under • $X_i \leftrightarrow X_i'$

$$\bullet + \leftrightarrow \cdot$$

- Widely used when you want to negate arbitrary logical function f

$$\begin{aligned} \text{e.g. } (a'b'+a'b+ab')' &= (a+b)(a+b')(a'+b) \\ &= aaa'+aab+ab'a'+ab'b+baa'+bab+bb'a'+bb'b \\ &= ab + ab = ab \\ \text{e.g. } ((a \cdot b)' \cdot (b' \cdot c)')' &= (a \cdot b) + (b' \cdot c) = a \cdot b + b' \cdot c \end{aligned}$$



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 2)

60

How to create CNF?

1. Gain DNF of negated function
 - Sum of "0" term in truth table
2. Negate function obtained in 1.

a	b	c		h	s	t	
0	0	0	$a'b'c'$	0	0	1	$h' = a'b'c' + a'bc' + ab'c' + abc$
0	0	1	$a'b'c$	1	1	1	↓
0	1	0	$a'bc'$	0	0	0	$h'' = (a'b'c' + a'bc' + ab'c' + abc)'$
0	1	1	$a'bc$	1	1	0	↓ De Morgan's law
1	0	0	$ab'c'$	0	0	0	$h = (a+b+c)(a+b'+c)$
1	0	1	$ab'c$	1	1	0	$(a'+b+c)(a'+b'+c')$
1	1	0	abc'	1	0	1	
1	1	1	abc	0	1	1	



Short exercise

- Show CNF of following logical function

a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1



Answer

- Show CNF of following logical function

$$f' = a'b'cd' + a'bcd + abcd'$$

$$f = f'' = (a'b'cd' + a'bcd + abcd)'$$

$$= (a+b+c+d)(a+b'+c'+d')(a'+b'+c'+d)$$

a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1



How to translate logical expression to sum of products or product of sums

$$h = a'(b'c + bc) + b'c' \quad \xrightarrow{\text{Negate}} \quad h' = (a'(b'c + bc) + b'c')'$$

Expand

$$h = a'b'c + a'bc + b'c'$$

Sum of products

Expand

$$h' = ab + ac + bc'$$

Negate

$$h'' = h = (ab + ac + bc)'$$

De Morgan's law

$$h = (a'+b')(a'+c')(b'+c)$$

Product of Sums

Note that the expansion route is not unique



Shannon's expansion

- A technique also used for translating logical expression to sum of products notation

$$f(x_1, x_2, \dots, x_n) = x_1' \cdot f(0, x_2, \dots, x_n) + x_1 \cdot f(1, x_2, \dots, x_n)$$

$$\begin{aligned} \text{e.g. } & (a'b' + a'b + ab)' \\ &= a'((1 \cdot b' + 1 \cdot b + 0 \cdot b)') + a((0 \cdot b + 0 \cdot b + 1 \cdot b)') \\ &\quad \text{Substitute } a=0 \qquad \text{Substitute } a=1 \\ &= a'((b' + b)') + a((b)') \\ &\quad = 1 \\ &= a'(0) + a(b'') = ab \end{aligned}$$



Short exercise

- Expand following function by Shannon's expansion and translate it to sum of products

$$f = \{(a \cdot b)' \cdot (b' \cdot c)'\}'$$



Answer

- Expand following function by Shannon's expansion and translate it to sum of products

$$f = \{(a \cdot b)' \cdot (b' \cdot c)'\}'$$

$$\begin{aligned} f &= a' \cdot \underbrace{\{(0 \cdot b)'\}}_{=1} \cdot (b' \cdot c)' + a \cdot \underbrace{\{(1 \cdot b)'\}}_{=b'} \cdot (b' \cdot c)' \\ &= a' \cdot \{(b' \cdot c)'\}' + a \cdot \{b' \cdot (b' \cdot c)'\}' \\ &= b' \cdot \underbrace{\{a' \cdot \{(1 \cdot c)'\}\}}_{=c} + a \cdot \underbrace{\{1 \cdot (1 \cdot c)'\}\}}_{=c} + b \cdot \underbrace{\{a' \cdot \{(0 \cdot c)'\}\}}_{=0} + a \cdot \underbrace{\{0 \cdot (0 \cdot c)'\}\}}_{=1} \\ &= b' \cdot (a' \cdot c + a \cdot c) + b \cdot a \\ &= \underbrace{(a' + a)}_{=1} \cdot b' \cdot c + a \cdot b = a \cdot b + b' \cdot c \end{aligned}$$



Equivalence of logical function

- There are equivalent logical expression in each logical function
 - In logical circuits design, there's possibility that it includes same circuits (= same logical expression)
 - > **Redundant!** (consume unnecessary silicon resources)
- How to check equivalence of them?
 - Checking on truth table is one method
 - The size of truth table is 2^n on n-value
 - Cogitated algorithm or data structure are required

-> Later Chap. 2



Quantity of logical function

- The logical function can be represented uniquely with truth table
- But there are 2^{2^n} of logical functions in n-value logical function

x	y	Q
0	0	?
0	1	?
1	0	?
1	1	?

} There are 2^4 possible outputs

x	y	Q
0	0	0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1
0	1	0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1
1	0	0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
1	1	0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1



Examples of 2-input logical function

- There's possible functions which are not named
- But usually, there's no use

x	y	AND $x \cdot y$	XOR $x \oplus y$	$(= x)$	$(= 0)$	$(= y)$	$(= 1)$
0	0	0	0	1	0	0	1
0	1	0	1	0	0	1	1
1	0	0	1	1	0	0	1
1	1	1	0	0	0	1	1



Quantity of logical function

- It increases dramatically in proportion to the number of values
 - $2^8 = 256$ in 3-value function
 - $2^{16} = 65536$ in 4-value function
 - $2^{32} = 4294967296$ in 5-value function
 - $2^{64} (\doteq 1.8 \times 10^{19})$ in 6-value function
 - Too hard to check all of them even if we use computer!
- Let's consider how to reduce number of logical functions



Symmetry logical function

The logical function is symmetry on x_i and x_j if outputs do not change under permutation of x_i and x_j

Example of symmetry: $f(x_1, x_2) = x_1 + x_2$ ($= x_2 + x_1$)

Example of not symmetry: $f(x_1, x_2) = x'_1 + x_2$ ($\neq x'_2 + x_1$)

- Quantity of logical function becomes 2^{n+1} if the function has **perfect symmetry**
 - The outputs do not change under permutation of all variables
 - e.g. $x'_1 \cdot x_2 \cdot x_3 + x_1 \cdot x'_2 \cdot x_3 + x_1 \cdot x_2 \cdot x'_3$

