

Hardware Design I Chap. 3

Minimization of two level logic

Computing Architecture Lab.
Hajime Shimada
E-mail: shimada@is.naist.jp

1

Outline

- Why we have to minimize logic size
 - Relationship between logical expression size and hardware
 - Delay and hardware cost on FET
- Minimizing logical expression method
 - Minimize on Boolean algebra
 - Karnaugh map
 - Quine-McCluskey algorithm




Relationship between logical expression and logical circuit

- The number of gates increase in proportion to the number of literals

- Assuming 2-input gates

- Do not consider cost of NOT gates
 
$$h = a'b'c + a'b'c + a'b'c + a'b'c' \quad \text{12 literals}$$




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

3

Multiple input CMOS NAND gates (1/2)

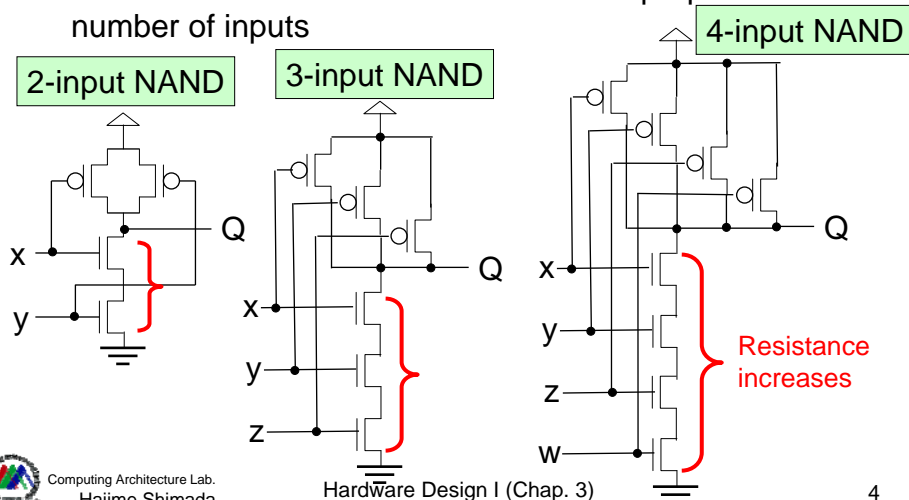- Serial connection of nMOS increases in proportion to the number of inputs





Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

4

Multiple input CMOS NAND gates (2/2)

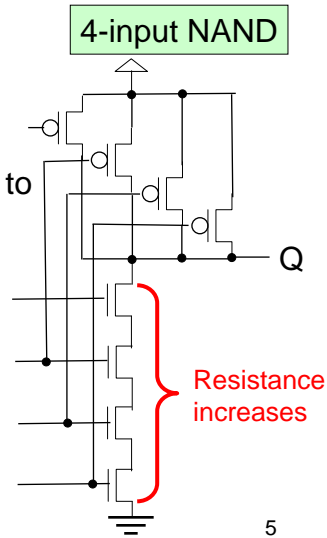 - Discharge speed of 4-input NAND is **half** of that of 2-input NAND
 - Resistance: $\times 2$
 - Current: $\times 1/2$
- Usually, we **extend gate width** of FET to reduce resistance
 - But it gives additional capacitance



Computing Architecture Lab.
Hajime Shimada


Hardware Design I (Chap. 3)

5

Gate width of FET


- We can choose several gate width of FET
 - We can choose channel width of FET
 - Enlarge channel width = Enlarge current conducting capacity
- But it gives additional capacitance of gate and diffusion area

Top view of nMOS FET

 

Capacitance $\times 3$

Gate width $\times 3$

 

Current $\times 3$
Used for
• Reduce resistance
• Drive many outputs




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

6

Operation delay of logic gates

- Voltage-time graph of NOT logic gate

 

- The gate delay slightly differs between semiconductor process technology
 - Shrinked technology is faster
 - Some techniques to improve transistor: strained silicon, SOI, etc...



Normalized delay of logic gates


- Gate delay differs with several parameters
 - Semiconductor process technology
 - Number of outputs ($\hat{=}$ gate width)
- **FO4 inverter delay**
 - The delay of the NOT gate which can drive 4 same NOT gate
 - An technology independent delay notation
 - e.g.
 - NOT gate which can drive 8 outputs: 1.2 FO4
 - NAND gate which can drive 4 outputs: 1.5 FO4
 - NAND gate which can drive 8 outputs: 1.7 FO4




Logic depth reduction with balanced tree

- We can reduce logic depth by balanced tree
 - Number of logic gates = (number_of_literals - 1)
 - Logic depth $\propto \log(\text{number_of_literals})$

a b c d e

 

Serial connection

 

Balanced tree



Why we have to create minimized circuit?

- To reduce silicon die size
 - Large circuit requires large silicon to place gates
- To create faster circuit
 - Large circuit increases capacitance and resistance which gives long charge/discharge time

Want to create smaller logical circuit



Want to create smaller logical expression



Example of combinational logic design

1. (Write truth table) ← - - - - Specification
2. Write logical expression ←
3. Simplify logical expression

a	b	cin	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{cout} = a' b \text{ cin} + a b' \text{ cin} + a b \text{ cin}' + a b \text{ cin}$$

$$\text{sum} = a' b' \text{ cin} + a' b \text{ cin}' + a b' \text{ cin}' + a b \text{ cin}$$

$$\text{cout} = (a' b + a b') \text{ cin} + a b$$

$$\text{sum} = \text{cin} (a' b' + a b) + \text{cin}' (a' b + a b')$$

Simplify
Including multi level circuit viewpoint
-> see Chap. 8



Outline

- Why we have to minimize logic size
 - Relationship between logical expression size and hardware
 - Delay and hardware cost on FET
- Minimizing logical expression method
 - Minimize on Boolean algebra
 - Karnaugh map
 - Quine-McCluskey algorithm



Minimize on Boolean algebra

- The rule used for simplification

- Idempotent: $a+a = a$
- Distributive: $(a+b) \cdot c = a \cdot c + b \cdot c$
- **Complements: $a+a' = 1$**
- Identity: $a \cdot 1 = a$

$$\begin{aligned} \text{e.g. } f &= a'bc + a'bc' + abc' + abc \\ &= a'bc + abc + a'bc' + abc' \\ &= \underbrace{(a'+a)}_{=1 \text{ (Complements)}}bc + \underbrace{(a'+a)}_{\text{Identity}}bc' = \underline{1bc} + \underline{1bc'} = \\ &= bc + bc' = b(c+c') = 1b = b \end{aligned}$$



Problems in minimizing on Boolean algebra

- Comparatively hard to determine what rule simplifies the logical expression
- Hard to determine what rule must be applied for final goal




- Usually, following method is widely used
 - Hand optimizing -> **Karnaugh map**
 - On EDA -> **Quine-McCluskey algorithm**



Outline of Karnaugh map (1/3)

 
- 2-dimension notation of truth table
 - Consecutive value can apply complements rule
 - With special order (gray code: 00, 01, 11, 10)
 - Group them with rectangle to apply complements rule
- e.g. $f = a'bc + a'bc' + abc' + abc = (a'b + a'b)$ or $(bc + bc')$



Outline of Karnaugh map (2/3)


- We can extend group size to apply complements rule further
 - The size of group must be 2^n

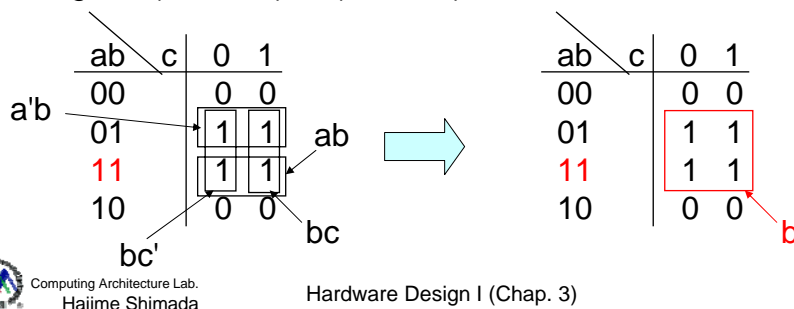e.g. $f = (a'b + ab)$ or $(bc + bc') = b$



Outline of Karnaugh map (3/3)

 - We can share a minterm between groups
 - e.g. $f = a'bc + a'bc' + abc' + abc + a'b'c = b + a'c$
 - If we input $(a,b,c)=(0,1,1)$, $f = b + a'c = \underline{1+1} = 1$
- You have to select least groups



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

17

Gray code

- A binary notation which only flips 1-bit in consecutive values

- Usual binary

0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000
 1-bit flip 2-bit 1-bit 3-bit 1-bit 2-bit 1-bit 4-bit

- Gray code

0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100
 1-bit flip 1-bit 1-bit 1-bit 1-bit 1-bit 1-bit 1-bit

- Assume mirrored order for lower bits after carry

0, 1, 11, 10, 110, 111, 101, 100, 1100




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

18

4-value Karnaugh map (1/3)

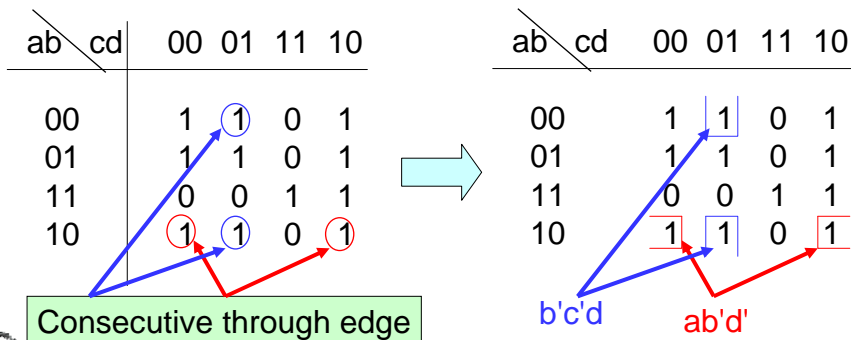- Please assume following edges are connected
 - Top edge and bottom edge
 - Left edge and right edge




Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

19

4-value Karnaugh map (2/3)

 - Example of 4-content group through edges
 - Watch out for a group which is consisted with 4 corners
- Consider 8-content group if it is possible



Computing Architecture Lab.
Hajime Shimada


Hardware Design I (Chap. 3)

20

4-value Karnaugh map (3/3)

- Considering least groups becomes more important

e.g. $f = a'c' + b'c' + cd' + abc$

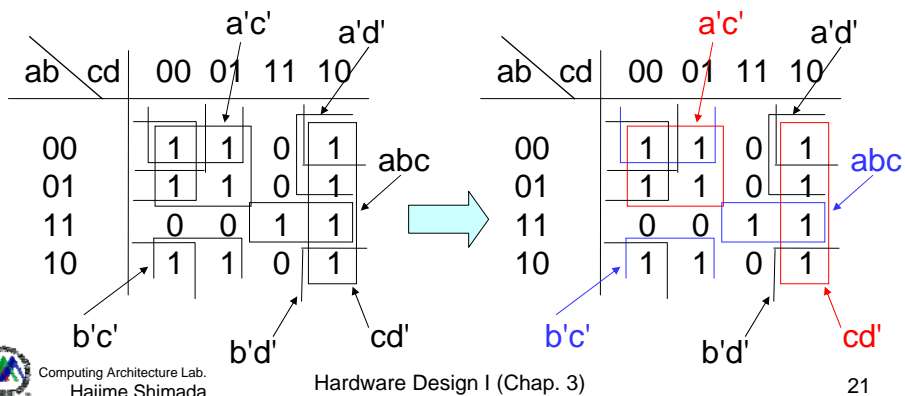

Prime implicant

- Prime implicant
 - A largest product term which covers "1" area on truth table
- Essential prime implicant
 - The prime implicant that covers some "1" area which has not covered by the other prime implicant
 - Must be chosen in first procedure when you are trying minimization of logical expression

Example of prime implicant

- $a'c'$, $b'c'$ and abc are selected as prime implicant
 - $a'bc'd$ is only covered by $a'c'$
 - $ab'c'd$ is only covered by $b'c'$
 - $abcd$ is only covered by abc
- Repeat similar operation
 - But sometimes it becomes **set cover problem** which is NP-complete problem

ab \ cd	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	0	0	1	1
10	1	1	0	1

Annotations: $a'c'$ (blue box), $b'c'$ (red box), abc (red box), $a'd'$ (black box), $b'd'$ (black box), cd' (black box).



5-value Karnaugh map

- The order of variables is as follows
 - 000, 001, 011, 010, 110, 111, 101, 100
- Assume that values which exist mirrored position from center are consecutive

ab \ cde	000	001	011	010	110	111	101	100
00								
01		1					1	
11		1					1	
10								


Annotations: $a'bc'd'e$ (red arrow), $a'bcd'e$ (blue arrow), $a'bd'e$ (blue arrow).

$$a'bc'd'e + a'bcd'e = a'bd'e$$



6-value Karnaugh map

 - Assume mirror to the center of vertical position
- The end of Karnaugh map
 - It requires another dimension if we increase values





Short Exercise

- Show simplified logical expression of following logical function with Karnaugh map

x y z	f(x, y, z)
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1



Answer

  

yz \ x	0	1
00	0	0
01	1	1
11	1	1
10	1	0

$$f(x, y, z) = x'y + z$$

xy \ z	0	1
00	0	1
01	1	1
11	0	1
10	0	1

zy \ x	0	1
00	0	0
01	1	0
11	1	1
10	1	1





Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

27

Outline

  

- Why we have to minimize logic size
- Karnaugh map
- Quine-McCluskey algorithm



Computing Architecture Lab.
Hajime Shimada

Hardware Design I (Chap. 3)

28

Quine-McCluskey algorithm

- An algorithm to get all prime implicant
 - Nearly brute force method
- Algorithm
 1. Translate minterm which outputs 1 to binary notation
 2. Sort with number of "1" in notation
 3. Create level ($i+1$) from level i
 - Select term pair which has only one different bit
 - Move it to level $i+1$ with translating differ point to *
 - Add flag to used term
 - Finish if there's no level $i+1$
 4. (Select essential prime implicant)



Example of Quine-McCluskey algorithm (1/3)

- Translate minterm which outputs 1 to binary notation
 - $a'b'c'$: 000
 - $a'bc$: 011
 - $ab'c$: 101
 - abc' : 110
 - abc : 111
- Treat above list as level 1

a b c	f
000	1
001	0
010	0
011	1
100	0
101	1
110	1
111	1



Example of Quine-McCluskey algorithm (2/3)

- Sort with number of "1" in notation
- Create level 2
 - Selected from different number of "1" notation group
 - We can use term redundantly

# of "1" is 0	000	→	Level 2	→	Level 1	→	Level 2
	011 x				000		*11
	101				011 x		*11
	110				101 x		1*1
	111 x				110 x		11*
					111 x		



Example of Quine-McCluskey algorithm (3/3)

- Not flagged values are prime implicants
- Check essential prime implicants with table
 - If minterm has only one "1" notation, the prime implicant is essential

Level 1	Level 2	Prime implicants	Minterms	*11	1*1	11*	000
000			000				1
011 x	*11		011	1			
101 x	1*1		101		1		
110 x	11*		110			1	
111 x			111	1	1	1	

Prime implicants

$$f = bc + ac + ab + a'b'c'$$



Example of prime implicant cannot be defined

- Sometimes it becomes set cover problem

- e.g. How to choose prime implicant to cover 0010, 0110, and 1010?
- See those topic in other lecture

	0*0*	*00*	0**0	*0*0	**10	111*
0000	1	1	1	1		
0001	1	1				
0010			1	1	1	
0100	1		1			
0101	1					
0110			1		1	
1111						1
1110					1	1
1000	1			1		
1001	1					
1010				1	1	

Annotations: A blue arrow points from the '1' in row 0100, column 0*0* to the '1' in row 0110, column 0*0*. A red arrow points from the '1' in row 0101, column 0*0* to the '1' in row 1110, column 0*0*. A red arrow points from the '1' in row 1000, column 0*0* to the '1' in row 1001, column 0*0*. A red arrow points from the '1' in row 1001, column 0*0* to the '1' in row 1110, column 0*0*. The word 'essential' is written in red next to the '1' in row 1110, column 0*0*.




Short exercise

- Show simplified logical expression of following logical function with Quine-McCluskey algorithm

x y z	f(x, y, z)
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1



Answer

 

	**1	01*
001	1	
010		1
011	1	1
101	1	
111	1	

Both of prime implicants are required

$$f(x, y, z) = x'y + z$$



How to minimize large hardware?

- Simplification ability of Karnaugh map and Quine-McCluskey algorithm are limited
 - Karnaugh map can treat until 6 variables
 - Quine-McCluskey algorithm can treat until around 30 values
 - Until around 10 variables in 1970's computer
- How to design large hardware with them?
 - Create module which has smaller inputs -> Chap. 4
 - Create large hardware by combining modules
- In practical use, we use MINI or Espresso -> Chap. 7

