

Hardware Design I Chap. 3 Minimization of two level logic

Computing Architecture Lab.
Hajime Shimada
E-mail: shimada@is.naist.jp

Outline

- Why we have to minimize logic size
 - Relationship between logical expression size and hardware
 - Delay and hardware cost on FET
- Minimizing logical expression method
 - Minimize on Boolean algebra
 - Karnaugh map
 - Quine-McCluskey algorithm




Relationship between logical expression and logical circuit

- The number of gates increase in proportion to the number of literals

○ Assuming 2-input gates


○ Do not consider cost of NOT gates
 
$$h = a'b'c + a'b'c + a'b'c + a'b'c \quad \text{12 literals}$$



Multiple input CMOS NAND gates (1/2)

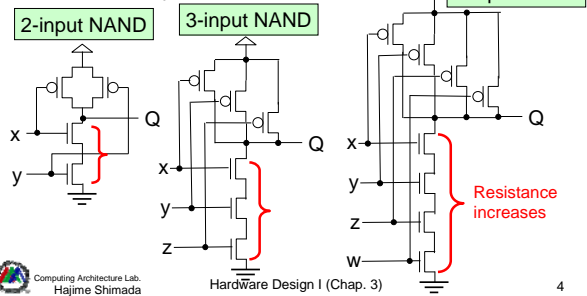- Serial connection of nMOS increases in proportion to the number of inputs




Multiple input CMOS NAND gates (2/2)

- Discharge speed of 4-input NAND is **half** of that of 2-input NAND

- Resistance: x2
- Current: x1/2


- Usually, we **extend gate width** of FET to reduce resistance

- But it gives additional capacitance

 


Gate width of FET

 - We can choose several gate width of FET
 - We can choose channel width of FET
 - Enlarge channel width = Enlarge current conducting capacity
- But it gives additional capacitance of gate and diffusion area



Operation delay of logic gates

- Voltage-time graph of NOT logic gate

 


- The gate delay slightly differs between semiconductor process technology
 - Shrinked technology is faster
 - Some techniques to improve transistor: strained silicon, SOI, etc...

Normalized delay of logic gates

- Gate delay differs with several parameters
 - Semiconductor process technology
 - Number of outputs ($\hat{=}$ gate width)
- **FO4 inverter delay**
 - The delay of the NOT gate which can drive 4 same NOT gate
 - An technology independent delay notation
 - e.g.
 - NOT gate which can drive 8 outputs: 1.2 FO4
 - NAND gate which can drive 4 outputs: 1.5 FO4
 - NAND gate which can drive 8 outputs: 1.7 FO4


Logic depth reduction with balanced tree

 - We can reduce logic depth by balanced tree
 - Number of logic gates = (number_of_literals - 1)
 - Logic depth \propto log (number_of_literals)



Why we have to create minimized circuit?

 - To reduce silicon die size
 - Large circuit requires large silicon to place gates
- To create faster circuit
 - Large circuit increases capacitance and resistance which gives long charge/discharge time



Example of combinational logic design

1. (Write truth table) ← Specification
2. Write logical expression
3. Simplify logical expression

a	b	cin	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

$cout = a' b' cin + a' b' cin' + a' b' cin' + a' b' cin$
 $sum = a' b' cin + a' b' cin' + a' b' cin' + a' b' cin$
 Simplify
 $cout = (a' b + a b') cin + a b$
 $sum = cin (a' b' + a b) + cin' (a' b + a b')$

Including multi level circuit viewpoint -> see Chap. 8

Outline

- Why we have to minimize logic size
 - Relationship between logical expression size and hardware
 - Delay and hardware cost on FET
- Minimizing logical expression method
 - Minimize on Boolean algebra
 - Karnaugh map
 - Quine-McCluskey algorithm

Minimize on Boolean algebra

- The rule used for simplification
 - Idempotent: $a+a = a$
 - Distributive: $(a+b) \cdot c = a \cdot c + b \cdot c$
 - Complements: $a+a' = 1$
 - Identity: $a \cdot 1 = a$

$$\begin{aligned}
 \text{e.g. } f &= a'bc + a'bc' + abc' + abc \\
 &= a'bc + abc + a'bc' + abc' \\
 &= (a'+a)bc + (a'+a)bc' = \underline{1}bc + \underline{1}bc' = \\
 &\quad = 1(\text{Complements}) \quad \text{Identity} \\
 &= bc + bc' = b(c+c') = 1b = b
 \end{aligned}$$

Problems in minimizing on Boolean algebra


- Comparatively hard to determine what rule simplifies the logical expression
- Hard to determine what rule must be applied for final goal



- Usually, following method is widely used
 - Hand optimizing -> **Karnaugh map**
 - On EDA -> **Quine-McCluskey algorithm**

Outline of Karnaugh map (1/3)

 
- 2-dimension notation of truth table
 - Consecutive value can apply complements rule
 - With special order (gray code: 00, 01, 11, 10)
 - Group them with rectangle to apply complements rule
- e.g. $f = a'bc + a'bc' + abc' + abc = (a'b + a'b) \text{ or } (bc + bc')$



Outline of Karnaugh map (2/3)


- We can extend group size to apply complements rule further
 - The size of group must be 2^n

 e.g. $f = (a'b + ab) \text{ or } (bc + bc') = b$



Outline of Karnaugh map (3/3)

 - We can share a minterm between groups
 - e.g. $f = a'bc + a'bc' + abc' + abc + a'b'c = b + a'c$
 - If we input $(a,b,c) = (0,1,1)$, $f = b + ac' = 1 + 1 = 1$
- You have to select least groups



Gray code

- A binary notation which only flips 1-bit in consecutive values

- Usual binary

0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000
 1-bit flip 2-bit 1-bit 3-bit 1-bit 2-bit 1-bit 4-bit

- Gray code


0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100
 1-bit flip 1-bit 1-bit 1-bit 1-bit 1-bit 1-bit 1-bit

- Assume mirrored order for lower bits after carry

0, 1, 11, 10, 110, 111, 101, 100, 1100


4-value Karnaugh map (1/3)

 - Please assume following edges are connected
 - Top edge and bottom edge
 - Left edge and right edge



4-value Karnaugh map (2/3)

 
- Example of 4-content group through edges
 - Watch out for a group which is consisted with 4 corners
- Consider 8-content group if it is possible



4-value Karnaugh map (3/3)

- Considering least groups becomes more important

e.g. $f = a'c' + b'c' + cd' + abc$

 


Prime implicant

- Prime implicant
 - A largest product term which covers "1" area on truth table
- Essential prime implicant
 - The prime implicant that covers some "1" area which has not covered by the other prime implicant
 - Must be chosen in first procedure when you are trying minimization of logical expression

 
Example of prime implicant

- $a'c'$, $b'c'$ and abc are selected as prime implicant
 - $a'bc'd$ is only covered by $a'c'$
 - $ab'c'd$ is only covered by $b'c'$
 - $abcd$ is only covered by abc
- Repeat similar operation
 - But sometimes it becomes **set cover problem** which is NP-complete problem



5-value Karnaugh map

 - The order of variables is as follows
 - 000, 001, 011, 010, 110, 111, 101, 100
- Assume that values which exist mirrored position from center are consecutive



6-value Karnaugh map

- Assume mirror to the center of vertical position
- The end of Karnaugh map
 - It requires another dimension if we increase values

def \ abc	000	001	011	010	110	111	101	100
000								
001	1						1	
011								
010								
110								
111								
101	1						1	
100								

Consecutive
 $a'b'cde'f$
 $+ ab'cde'f$
 $= b'cde'f$

$b'ce'f$

Short Exercise

- Show simplified logical expression of following logical function with Karnaugh map

x y z	f(x, y, z)
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Answer

yz \ x	0	1
00	0	0
01	1	1
11	1	1
10	1	0

$f(x, y, z) = x'y + z$

$x'y$

xy \ z	0	1
00	0	1
01	1	1
11	0	1
10	0	1

$x'y$

z

zy \ x	0	1
00	0	0
01	1	0
11	1	1
10	1	1

$x'y$

z

Outline

- Why we have to minimize logic size
- Karnaugh map
- Quine-McCluskey algorithm

Quine-McCluskey algorithm

- An algorithm to get all prime implicant
 - Nearly brute force method
- Algorithm
 - Translate minterm which outputs 1 to binary notation
 - Sort with number of "1" in notation
 - Create level ($i+1$) from level i
 - Select term pair which has only one different bit
 - Move it to level $i+1$ with translating differ point to *
 - Add flag to used term
 - Finish if there's no level $i+1$
 - (Select essential prime implicant)

Example of Quine-McCluskey algorithm (1/3)


- Translate minterm which outputs 1 to binary notation

a b c	f
000	1
001	0
010	0
011	1
100	0
101	1
110	1
111	1

- Treat above list as level 1

 Example of Quine-McCluskey algorithm (2/3)

- Sort with number of "1" in notation
- Create level 2
 - Selected from different number of "1" notation group
 - We can use term redundantly



Example of Quine-McCluskey algorithm (3/3)

- Not flagged values are prime implicants
- Check essential prime implicants with table
 - If minterm has only one "1" notation, the prime implicant is essential

Level 1	Level 2	Prime implicants	*11	1*1	11*	000
000	000	Minterms				1
011 x	*11	011	1			
101 x	1*1	101		1		
110 x	11*	110			1	
111 x	Prime implicants	111	1	1	1	

$f = bc + ac + ab + a'b'c'$

Example of prime implicant cannot be defined

- Sometimes it becomes set cover problem
 - e.g. How to choose prime implicant to cover 0010, 0110, and 1010?
 - See those topic in other lecture


	0*0*	*00*	0**0	*0*0	**10	111*
0000	1	1	1	1		
0001	1	1				
0010			1	1	1	
0100	1		1			
0101	1					
0110			1	1	1	
1111						1
1110				1	1	
1000			1	1		
1001			1			
1010				1	1	

Short exercise

- Show simplified logical expression of following logical function with Quine-McCluskey algorithm

x y z	f(x, y, z)
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Answer

 

	**1	01*	
001	1		
010		1	
011	1	1	
101	1		
111	1		

Both of prime implicants are required

$f(x, y, z) = x'y + z$

How to minimize large hardware?

- Simplification ability of Karnaugh map and Quine-McCluskey algorithm are limited
 - Karnaugh map can treat until 6 variables
 - Quine-McCluskey algorithm can treat until around 30 values
 - Until around 10 variables in 1970's computer
- How to design large hardware with them?
 - Create module which has smaller inputs -> Chap. 4
 - Create large hardware by combining modules
- In practical use, we use MINI or Espresso -> Chap. 7